# Thermocouple Interfacing with AVR ATmega16/ATmega32

# **Overview of Thermocouple**






Thermocouple

A thermocouple consists of two different conductors forming an electrical junction at different temperatures.

Due to thermo effect, thermocouples produce a voltage which is dependent on temperature.

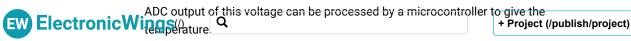Temperature can be found out from this voltage.






Platforms (/explore)

Projectanore informat@alestaThermocouple and how to use it, refer to the topic (/projecta)ocouple (http://projecta)ocouple (http://projecta)ocoupl

For information about ADC in ATmega16 and how to use it, refer to the topic **ADC in AVR ATmega16/ATmega32** (http://electronicwings.com/avr-atmega/atmega1632-adc) in the ATmega inside section.
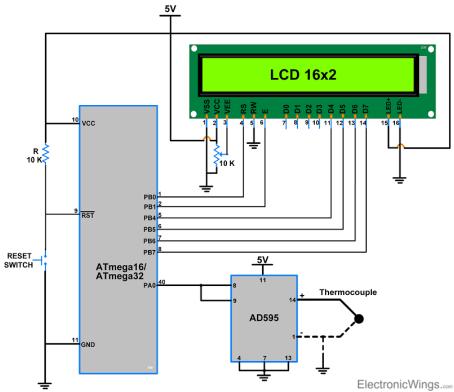
# Connection Diagram of Thermocouple with ATmega16/32

• The complete interfacing diagram of the thermocouple is shown in figure below.



Interfacing Thermocouple With ATmega16/ATmega32

#### **AD595**


- AD595 is a complete instrumentation amplifier (Monolithic Thermocouple Amplifiers) with a Cold Junction Compensation.
- AD595 is compatible with a K-type thermocouple, while AD594 is compatible with a J-type thermocouple.
- It combines ice point reference with the pre-calibrated amplifier to produce a high-level output (10mV/°C) directly from the thermocouple output.
- AD595 gain trimmed to match transfer characteristic of K-type thermocouple at 25°C. The output of a K-type thermocouple in this temperature range is 40.44uV/°C.
- The resulting gain for AD595 is 247.3 (10mV/°C divided by 40.44uV/°C).



Platforms (/explore) Projects input. Contests (/projects) The output of AD595 is (/contests)

AD595 Output = (Type K Voltage + 11 uV) x 247.3

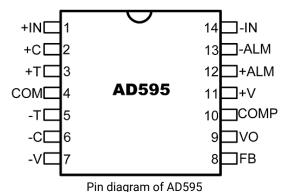• The IC AD595 pin diagram is shown in the figure below.



**Note:** if you connect +5 volt and ground to the AD595 you can measure the temperature 0°C to +300°C, for more information refers to AD595 datasheet.

### **Programming for Thermocouple**

#### Steps:

- 1. Initialize the ADC and LCD.
- 2. Take the data from the AD595 instrumentation amplifier.
- 3. Convert the ADC value into °C using the below formula,

$$C = rac{( ext{adcValue} * 4.88) - 0.0027}{10}$$

Why 0.0027 subtracted in the above formula

AD595 provides output as follows,

#### AD595 Output = (Type K Voltage + 11 uV) x 247.3


The above formula shows AD595 provides output with amplified offset voltage.
 So, we have to eliminate the total offset voltage (11 uV \* 247.3) to get an accurate temperature value.

**Note:** 11 uV is an offset voltage of the IC AD595 instrumentation amplifier for K-type thermocouple.

4. Display Temperature on 16x2 LCD.

# Thermocouple Code for ATmega16/32

/\* Vref: Avcc, ADC channel: 0 \*/

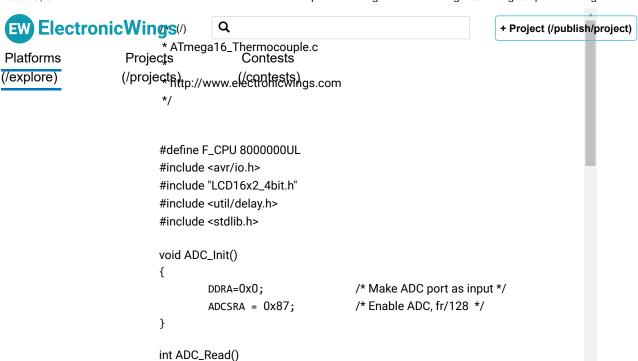

# Video of Temperature Measurement using Atmega16/32

ADMUX = 0x40;







mouser.in?

(https://www.



Platforms (/explore)

Projects (/projects)

Contests (/contests)

# Components Used

utm\_source=el
ectronicswing
Powered By
s&utm\_mediu
m=display&ut
m\_campaign=
mousercomponentsli
sting&utm\_co
ntent=0x0)

ATmega 16
ATmega 16
X 1

■ Datasheet (/componen ts/atmega-16/1/datash eet)

Atmega32 X 1

■ Datasheet (/componen ts/atmega3 2/1/datashe et)







mouser.in?

ntent=0x0)

(https://www.



Platforms (/explore)

Projects (/projects)

Contests (/contests)

# **Components Used**

utm\_source=el
ectronicswing
Powered By s&utm\_mediu
m=display&ut
m\_campaign=
mousercomponentsli
sting&utm\_co

om/ProductDetail/Ada fruit/270? qs=GURawfaeGuACM a%252Bo9T3i3g%3D% 3D&utm\_source=electr onicswings&utm\_medi um=display&utm\_cam paign=mousercomponentslisting&ut

(https://www.mouser.c

Datasheet (/componen ts/k-typethermoc ouple-glass-braid-insulated/1/

m\_content=0x0)

insulated/1/datasheet)

(https://www.mouser.com/ProductDetail/Analog-Devices/AD595ADZ?

qs=NmRFExCfTkG5hT KeP7qMog%3D%3D&u tm\_source=electronics wings&utm\_medium=d isplay&utm\_campaign =mouser-

componentslisting&ut m\_content=0x0)

Datasheet (/componen ts/ad595- thermocoupl er- amplifier/1/ datasheet)


#### K TypeThermocouple Glass Braid Insulated

K TypeThermocouple Glass Braid Insulated

X 1

#### **AD595 THERMOCOUPLER AMPLIFIER**

AD595 THERMOCOUPLER AMPLIFIER

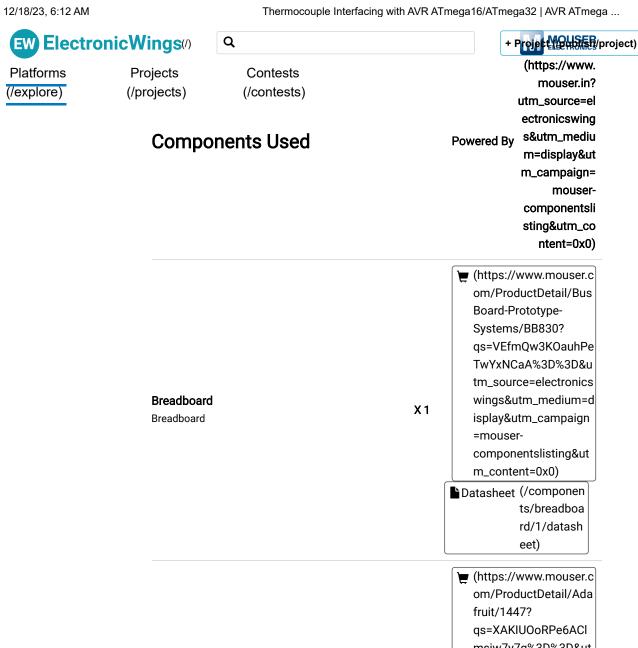

LCD16x2 Display LCD16x2 Display

X 1

msjw7y7g%3D%3D&ut m\_source=electronics wings&utm\_medium=d isplay&utm\_campaign =mousercomponentslisting&ut m\_content=0x0)

### **Downloads**

Atmega Thermocouple Project file

Dow (/api/download/platf nloa orm-attachment/356) d



+ Project (/publish/project)







18bec032

plz. make a code for interfacing RTD PT100 to micro controller (AVR/PIC).

(/users/18bec032/profile) 2020-05-13 16:25:06

Reply Like 1 ₺

can you give me the code in assembly level language used for AT89c51 Reply Like

About Us (/about)
Business Offering (/businessservices)
Host Platform (/launchplatform)

Facebook(https://www.facebook.com/electronicwings)
LinkedIn(https://www.linkedin.com/company/electronicwin

:

platform)

Contact Us (/contactus) Youtube(https://www.youtube.com/channel/UCNdqkukBtk4

Connect On:

(https://www.instagram.com/electronicwings\_collinstagram iqshid=1cip10jijttko)

Terms of Service (/terms-ofservice) Cookies Policy (/cookie-policy)

Privacy Policy (/privacy-policy)

ElectronicWings © 2023